

**CHAPTER NO. 13(CURRENT ELECTRICITY)**

**Question 13.1:-** How many electrons pass through an electric bulb in one minute if the 300 mA current is passing through it?

**Solution:-** Current =  $I = 300 \text{ mA} = 300 \times 10^{-3} \text{ A} = 0.3 \text{ A}$

Time = 1 minute = 60 s

Current =  $I = \text{Charge}/\text{time} = q/t$

$q = It = (0.3)(60) = 1.8 \text{ C}$

We know that total charge passing through the bulb in terms of electronic charge  $e$  is  $q = ne$ .

We can say that  $q = ne$

$$n = q/e = \frac{1.8}{1.60 \times 10^{-19}} = 1.12 \times 10^{19}$$

**$n = 1.12 \times 10^{19}$**

**Question 13.2:-** A charge of 90 C passes through a wire in 1 hour and 15 minutes. What is the current in the wire?

**Solution:-** Charge =  $q = 90 \text{ C}$

Time =  $t = 1 \text{ hour } 15 \text{ minutes} = 75 \text{ minutes} = 75 \times 60 \text{ s} = 4500 \text{ s}$

Current =  $I = \text{Charge}/\text{time} = q/t$

$I = 90/4500 = 1/50 \text{ A}$

$I = 0.02 \text{ A}$

**$I = 20 \text{ mA}$**

**Question 13.3:-** Find the equivalent resistance of the circuit, total current drawn from the source and the current through each resistor.

**Solution:-** EMF of battery =  $V = 6 \text{ V}$

We can see that  $R_1$  and  $R_2$  are connected in parallel. The parallel combination of  $R_1$  and  $R_2$  is connected in series with  $R_3$ .

We can solve parallel combination as  $\frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2}$

$$R_{12} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(6)(6)}{6+6} = 3 \Omega$$


$R_T = R_{12} + R_3 = 3 + 3$

**$R_T = 6 \Omega$**

The current drawn from the source is  $I_T = V/R_T = 6/6$

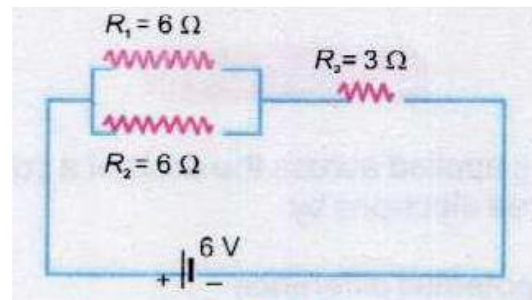**$I_T = 1 \text{ A}$**

Since  $R_1$  and  $R_2$  are connected in parallel, voltage drop is same across them but current coming from the source  $V$  is divided in two part  $I_1$  and  $I_2$ .



$\therefore R_{12}$  is in series with  $R_3$

The potential drop across parallel combination of  $R_1$  and  $R_2 = V_{12} = I_T R_{12} = (1)(3) = 3 \text{ V}$

Current through  $R_1 = I_1 = V_{12}/R_1 = 3/6$

$$\underline{I_1 = 0.5 \text{ A}}$$

Current through  $R_2 = I_2 = V_{12}/R_2 = 3/6$

$$\underline{I_2 = 0.5 \text{ A}}$$

The current passing through  $R_1$  and  $R_2$  is added up to pass through  $R_3$ .

Current through  $R_3 = I_3 = I_T = I_1 + I_2$

$$\underline{I_3 = 1 \text{ A}}$$

**Question 13.4:-** A rectangular bar of iron is 2.0 cm by 2.0 cm in cross section and 40 cm long.

Calculate its resistance if the resistivity of iron is  $11 \times 10^{-8} \Omega \text{ m}$ .

**Solution:-** Resistivity of iron  $= \rho = 11 \times 10^{-8} \Omega \text{ m}$

Length of iron bar  $= 40 \text{ cm} = 0.4 \text{ m}$

Width of iron bar  $= W = 2.0 \text{ cm} = 0.02 \text{ m}$

Breadth of iron bar  $= B = 2.0 \text{ cm} = 0.02 \text{ m}$

Area of cross section  $= A = \text{Width} \times \text{Breadth} = W \times B = 0.02 \times 0.02 = 4 \times 10^{-4} \text{ m}^2$

Resistance  $= R = \rho \frac{L}{A} = (11 \times 10^{-8}) \left( \frac{0.4}{4 \times 10^{-4}} \right)$

$$\underline{R = 1.1 \times 10^{-4} \Omega}$$

**Question 12.5:-** The resistance of an iron wire at  $0^\circ \text{C}$  is  $1 \times 10^4 \Omega$ . What is the resistance at  $500^\circ \text{C}$  if the temperature coefficient of resistance of iron is  $5.2 \times 10^{-3} \text{ K}^{-1}$ ?

**Solution:-** Temperature coefficient of resistance of iron  $= \alpha = 5.2 \times 10^{-3} \text{ K}^{-1}$

Resistance at  $0^\circ \text{C} = R_0 = 1 \times 10^4 \Omega$

Initial temperature  $= t_1 = 0^\circ \text{C} = 273 \text{ K}$

Final temperature  $= t_2 = 500^\circ \text{C} = 773 \text{ K}$

Rise in temperature  $= t = t_2 - t_1 = 773 - 273 = 500 \text{ K}$

We know that  $\alpha = \frac{R_t - R_0}{R_0 t}$

Rearranging gives  $R_t = R_0 (1 + \alpha t)$

$R_t = (1 \times 10^4) [1 + (5.2 \times 10^{-3})(500)] = (1 \times 10^4) (1 + 2.6)$

$$\underline{R_t = 3.6 \times 10^4 \Omega}$$


**Question 13.6:-** Calculate the terminal potential difference of each of cells in circuit of figure.

**Solution:-** EMF of first cell  $= E_1 = 24 \text{ V}$

Internal resistance of first cell  $= r_1 = 0.10 \Omega$

EMF of second cell  $= E_2 = 6 \text{ V}$

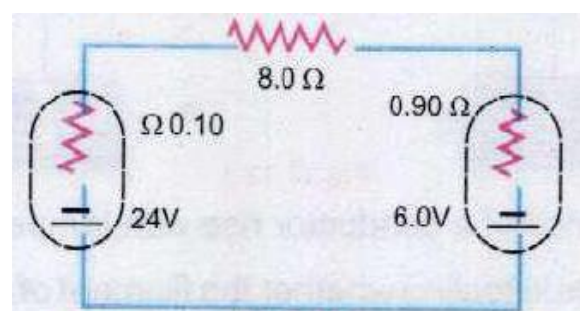Internal resistance of second cell  $= r_2 = 0.90 \Omega$



External resistance =  $R = 8.0 \Omega$

EMF of first cell =  $E_1 = 24 \text{ V}$

Internal resistance of first cell =  $r_1 = 0.10 \Omega$

In the given circuit, both batteries oppose each other as positive terminals of both are connected to each other. The circuit is a series circuit. The current is being supplied by the first battery  $E_1$  and second battery is being charged by current of first battery.

$$\text{Current supplied by the first cell} = I = \frac{E_1 - E_2}{r_1 + r_2 + R} = \frac{24 - 6}{0.10 + 0.90 + 8.0}$$

$$I = 2 \text{ A}$$

$$\text{Terminal potential difference of first cell} = V_1 = E_1 - I r_1 = 24 - (2)(0.10)$$

$$\underline{V_1 = 23.8 \text{ V}}$$

$$\text{Terminal potential difference of first cell} = V_2 = E_2 - I r_2 = 6 + (2)(0.90)$$

$$\underline{V_2 = 7.8 \text{ V}}$$

**Question 13.7:-** Find the current which flows in all the resistances of the circuit of figure.

**Solution:-** First of all, label all the branches of circuit. Assign current to  $R_1$  and  $R_2$  with the arrow symbol showing the direction of conventional current.

$$\text{EMF of first cell} = E_1 = 9.0 \text{ V}$$

$$\text{EMF of second cell} = E_2 = 6.0 \text{ V}$$

We can easily see this is a parallel circuit.

Since,  $R_1$  and  $E_1$  are connected in parallel:

$$\text{Current through } R_1 = I_1 = E_1 / R_1 = 9.0 / 18$$

$$\underline{I_1 = 0.5 \text{ A (Direction of conventional current is from B to A)}}$$

We can also see that  $E_1$  is in parallel with series combination of  $R_2$  and  $E_2$ , so we can say that

$$E_1 = I_2 R_2 - E_2$$



$$9.0 = I_2 (12) - 6$$

$$I_2 = \frac{9+6}{12}$$

$$\underline{I_2 = 1.25 \text{ A (Direction of conventional current is from B to A)}}$$

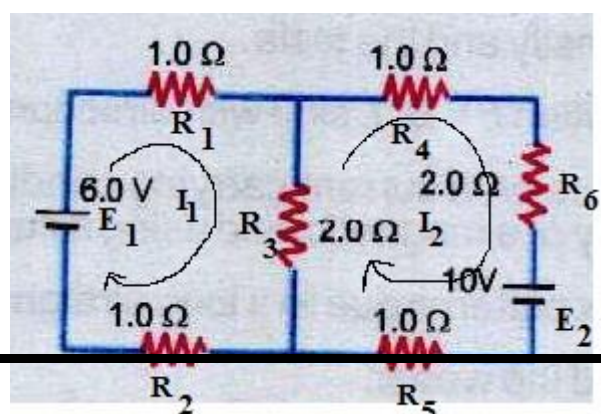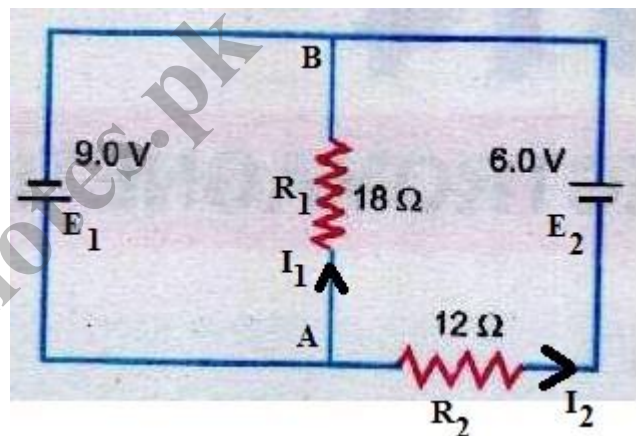**Question 13.8:-** Find the current and power dissipated in each resistance of the circuit, shown in figure.

**Solution:-** First of all, label all the branches of circuit. There are two closed conducting paths i.e. loops in the circuit. We have



assigned current to both loops in clockwise direction.

We will write the equations of both loops by using Kirchhoff's second rule and solve them.

**LOOP 1:**

$$-I_1 R_1 - (I_1 - I_2) R_3 - I_1 R_3 + E_1 = 0$$

Put values of  $R_1, R_2, R_3$  and  $E_1$ .

$$6 = 4 I_1 - 2 I_2$$

$$3 = 2 I_1 - I_2 \text{ ----- Eq. (1)}$$

**LOOP 2:**

$$-I_2 R_4 - I_2 R_6 - E_2 - I_2 R_5 - (I_2 - I_1) R_3 = 0$$

Put values of  $R_3, R_4, R_5, R_6$  and  $E_2$ .

$$10 = 2 I_1 - 6 I_2$$

$$5 = I_1 - 3 I_2 \text{ ----- Eq. (2)}$$

We can solve these equations algebraically.

Multiply Eq. (2) with 3 and subtract it from Eq. (1) gives the value of  **$I_1 = 0.8 \text{ A}$**

Put the value of  $I_1 = 0.8 \text{ A}$  in Eq. (1) gives  $3 = 2 (0.8) - I_2$

**$I_2 = -1.4 \text{ A}$**  (The negative sign indicates that actual current is flowing opposite to the assigned direction)

**Current through  $R_1$  and  $R_2 = I_1 = 0.8 \text{ A}$  (Clockwise direction)**

**Current through  $R_3 = I_1 - I_2 = 0.8 - (-1.4) = 2.2 \text{ A}$  (Clockwise direction)**

**Current through  $R_4, R_5$  and  $R_6 = |I_2| = 1.4 \text{ A}$  (Anticlockwise direction)**

**Power drop across  $R_1$  and  $R_2 = I_1^2 R_1^2 = I_1^2 R_2^2 = (0.8)^2 (1) = 0.64 \text{ W}$**

**Power drop across  $R_3 = (I_1 - I_2)^2 R_3^2 = (2.2)^2 (2) = 9.68 \text{ W}$**

**Power drop across  $R_4$  and  $R_5 = I_2^2 R_4^2 = I_2^2 R_5^2 = (1.4)^2 (1) = 1.96 \text{ W}$**

**Power drop across  $R_6 = I_2^2 R_6 = (1.4)^2 (2) = 3.92 \text{ W}$**

**CONVENTIONS**

RESISTOR	EMF SOURCE
a) Voltage change across a resistor is positive if traversed against the direction of current.	a) Voltage change across an emf source is positive if traversed from negative to positive terminal.
b) Voltage change across a resistor is negative if traversed in the direction of current.	b) Voltage change across an emf source is negative if traversed from positive to negative terminal.