

CHAPTER NO. 18(ELECTRONICS)

Question 18.1:- The current flowing into the base of a transistor is $100 \mu\text{A}$. Find its collector current I_C , its emitter current I_E and the ratio I_C/I_E , if the value of current gain β is 100.

Solution:- Base current = $I_B = 100 \mu\text{A} = 100 \times 10^{-6} \text{ A} = 0.1 \text{ mA}$

Current gain = $\beta = 100$

Collector current = $I_C = \beta I_B = (100) (100 \times 10^{-6})$

$I_C = 1 \times 10^{-2} \text{ A} = 10 \times 10^{-3} \text{ A}$

$I_C = 10 \text{ mA}$

Emitter current = $I_E = I_C + I_B = 10 \text{ mA} + 0.1 \text{ mA}$

$I_E = 10.1 \text{ mA}$

The ratio of currents = $I_C/I_E = 10 \text{ mA}/10.1 \text{ mA}$

$I_C/I_E = 0.99$

Question 18.2:- Fig.P.18.2 shows a transistor which operates a relay as the switch S is closed. The relay is energized by a current of 10 mA. Calculate the value of R_B which will just make the relay to operate. The current gain β of the transistor is 200. When the transistor conducts, its V_{BE} can be assumed to be 0.6 V.

Solution:- Power supply voltage = $V_{CC} = 9 \text{ V}$

Relay current = $I_C = 10 \text{ mA} = 0.01 \text{ A}$

Current gain = $\beta = 200$

Potential drop between base and emitter = $V_{BE} = 0.6 \text{ V}$

We can find I_B by using the relation $I_C = \beta I_B$

$I_B = I_C/\beta = 0.01/200 = 0.00005 \text{ A} = 50 \times 10^{-6} \text{ A} = 50 \mu\text{A}$

Applying Kirchhoff's second rule to base loop gives $V_{CC} = I_B R_B + V_{BE}$

$R_B = (V_{CC} - V_{BE})/I_B = (9 - 0.6)/(50 \times 10^{-6})$

$R_B = 0.168 \times 10^6 \Omega = 168 \times 10^3 \Omega$

$R_B = 168 \text{ k}\Omega$



Question 18.3:- In circuit (Fig.P.18.3), there is negligible potential drop between B and E, if β is 100. Calculate (i) base current (ii) collector current (iii) potential drop across R_C (iv) V_{CE} .

Solution:- Current gain = $\beta = 100$

Base resistance = $R_B = 800 \text{ k}\Omega = 800 \times 10^3 \Omega$

Collector resistance = $R_C = 1 \text{ k}\Omega = 1 \times 10^3 \Omega$

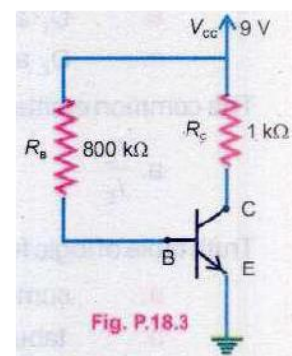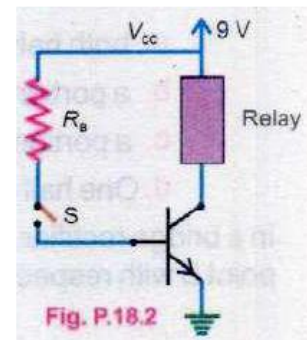Power supply voltage = $V_{CC} = 9 \text{ V}$



Potential drop between base and emitter = $V_{BE} = 0 \text{ V}$

(i) Applying Kirchhoff's second rule across base loop gives $V_{CC} = I_B R_B + V_{BE}$

$$I_B = (V_{CC} - V_{BE})/R_B$$

$$I_B = (9 - 0)/(800 \times 10^3) = 0.01125 \times 10^{-3} \text{ A}$$

$$I_B = 11.25 \times 10^{-6} \text{ A}$$

$$\underline{I_B = 11.25 \mu\text{A}}$$

(ii) Collector current = $I_C = \beta I_B = (100) (11.25 \times 10^{-6}) = 1.125 \times 10^{-3} \text{ A}$

$$\underline{I_C = 1.125 \text{ mA}}$$

(iii) Potential drop across $R_C = I_C R_C = (1.125 \times 10^{-3}) (1 \times 10^3)$

$$\underline{\text{Potential drop across } R_C = 1.125 \text{ V}}$$

(iv) Applying Kirchhoff's second rule across collector loop gives $V_{CC} = I_C R_C + V_{CE}$

$$V_{CE} = V_{CC} - I_C R_C = 9 - (1.125 \times 10^{-3}) (1 \times 10^3)$$

$$V_{CE} = 9 - 1.125$$

$$\underline{V_{CE} = 7.875 \text{ V}}$$

Question 18.4:- Calculate the output of the op-amp circuit shown in Fig.P.18.4.

Solution:- $R_2 = 20 \text{ k}\Omega$

$$R_1 = 10 \text{ k}\Omega$$

$$R_1' = 4 \text{ k}\Omega$$

$$V_1 = +5 \text{ V}$$

$$V_2 = -2 \text{ V}$$

There are two input voltages V_1 and V_2 . We have to find output voltages due to both input separately and then them.

In an amplifier, $V_{out} = G V_{in}$ where G is voltage gain. For op-amp in inverting configuration, $G = -R_2/R_1$

$$V_{out} = (-R_2/R_1) V_1 + (-R_2/R_1') V_2 = (-20/10) (5) + (-20/4)(-2)$$

$$V_{out} = -10 + 10$$

$$\underline{V_{out} = 0 \text{ V}}$$

Question 18.5:- Calculate the gain of non-inverting amplifier shown in Fig.P.18.5.

Solution:- $R_2 = 40 \text{ k}\Omega$

$$R_1 = 10 \text{ k}\Omega$$

$$\text{Gain on non-inverting amplifier} = G = 1 + \frac{R_2}{R_1}$$

$$G = 1 + (40/10) = 1 + 4$$

$$\underline{G = 5}$$

